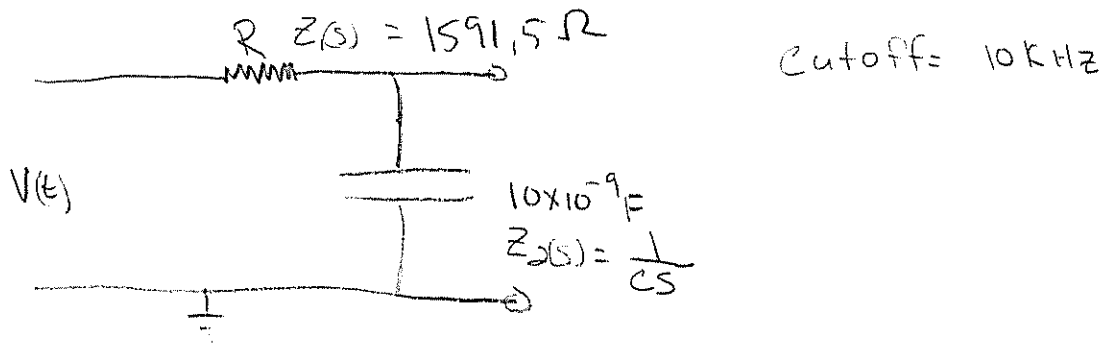


Problem 1.



$$H(s) = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R} = \frac{1}{1 + RCs} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

From notes:

$$\omega_c = 2\pi f = 20 \times 10^3 \pi$$

$$\frac{1}{RC} = 20 \times 10^3 \pi \Rightarrow R = \frac{1}{(20 \times 10^3 \pi)(10 \times 10^{-9})} = 1591.5 \Omega$$

a) see graph

$$b) \frac{1}{RC} = \frac{1}{(1591.5)(10 \times 10^{-9})} = 62834 \quad -10 \text{ dB} = 0.316$$

$$|H(j\omega)| = \frac{62834}{\sqrt{\omega^2 + 62834^2}} = 0.316$$

$$\omega = 188653 \quad f = \frac{\omega}{2\pi}$$

$$f = 29.933 \text{ kHz} \approx 30 \text{ kHz}$$

$$c) \angle H(j\omega) = \angle \text{Top} - \angle \text{Bottom} \Rightarrow 0 - \tan^{-1} \frac{\omega}{62834}$$

$$45 = \tan^{-1} \frac{\omega}{62834}$$

$$\omega \approx 62834 \quad f = \frac{\omega}{2\pi}$$

$$f = 10 \text{ kHz}$$

## Problem #2

a)  $Q = .707$  (best  $Q$  for 2<sup>nd</sup> order High Pass)

Cut off =  $7000\pi$  rad/sec because  $2000\pi$  rad/sec is below cut off and  $10,000\pi$  rad/sec +  $20,000\pi$  rad/sec are above the cut off

b) assume  $C = 10$  nF

$$\omega_c = \frac{1}{\sqrt{LC}} \Rightarrow 5000\pi = \frac{1}{\sqrt{L \cdot 10 \times 10^{-9}}}$$

$$L = .405 \text{ H}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow .707 = \frac{1}{R} \sqrt{\frac{.405}{10 \times 10^{-9}}} \approx 9k$$

$$c) H(s) = \frac{s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \Rightarrow \frac{(j\omega)^2}{(j\omega)^2 + j\omega \frac{\omega_0}{Q} + \omega_0^2}$$

$$|H(j\omega)| = \frac{|\omega^2|}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q}\omega\right)^2}}$$


| $\omega$    | $ H(j\omega) $ | $\angle H(j\omega)$ |
|-------------|----------------|---------------------|
| $2000\pi$   | .158           | .768                |
| $5000\pi$   | .707           | -                   |
| $10,000\pi$ | .970           | -.6399              |
| $20,000\pi$ | .998           | -.9504              |

$$\angle H(j\omega) = \angle \text{top} - \angle \text{bottom}$$

$$= \tan^{-1}(0) - \tan^{-1} \frac{\omega_0^2 - \omega^2}{\frac{\omega_0}{Q}\omega}$$

$$y_{ss} = .0158 \cos(2000\pi t + 1.82) + .970 \cos(10000\pi t - .6399) + 1.098 \cos(20000\pi t - .9504)$$

Problem #3  $100 \times 10^{-12}$  a+b

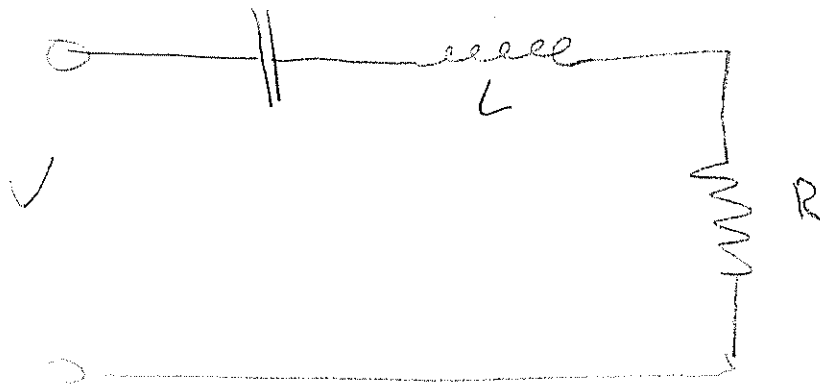


$$Q = \frac{\omega_0}{\text{Band width}} = \frac{100,000}{10,000} = 10$$

Center = 100 kHz

$$2 \cdot 100,000 \pi = \frac{1}{\sqrt{L \cdot 100 \times 10^{-12}}} \quad L = 0.2533$$
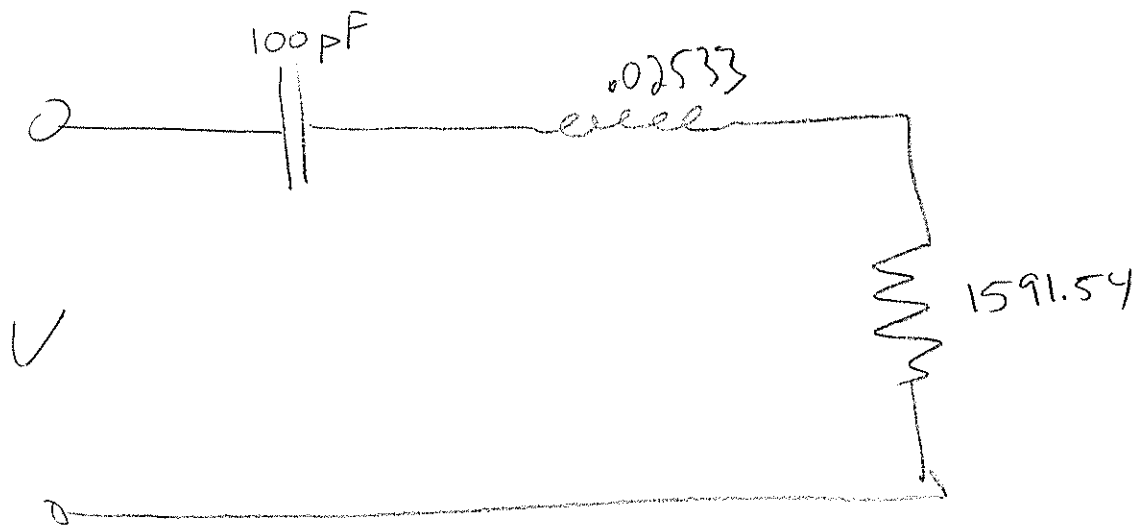
$$10 = \frac{1}{R} \sqrt{\frac{0.2533}{100 \times 10^{-12}}} \quad R = 1591.54$$



Problem 3 part c

$$100 \times 10^{-12} \times .80 =$$

$$100 \times 10^{-12} \times .90 =$$

$$100 \times 10^{-12} \times .95 =$$

$$100 \times 10^{-12} \times 1.05 =$$

$$100 \times 10^{-12} \times 1.1 =$$

$$100 \times 10^{-12} \times 1.2 =$$

$$\underline{C}$$

$$8 \times 10^{-11}$$

$$9 \times 10^{-11}$$

$$9.5 \times 10^{-11}$$

$$1.05 \times 10^{-10}$$

$$1.1 \times 10^{-10}$$

$$1.2 \times 10^{-10}$$

$$\underline{\omega}$$

$$702486$$

$$662310$$

$$644645$$

$$613180$$

$$599682$$

$$573577$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$L = .02533$$

Center f

$$111804$$

$$105410$$

$$102598$$

$$97590.6$$

$$95346.9$$

$$91287.6$$

$$f = \frac{\omega}{2\pi}$$

Q

$$11.18$$

$$10.54$$

$$10.25$$

$$9.76$$

$$9.53$$

$$9.13$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$R = 1591.54$$

$$L = .02533$$