

(a)

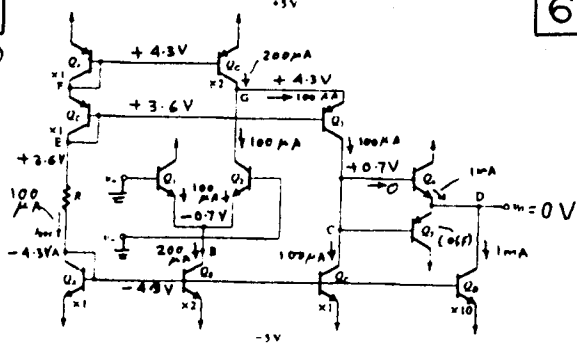


Fig. P6.122 DC Analysis

$$R = \frac{3.6 - (-4.3)}{100 \mu A} = 79 \text{ k}\Omega$$

Node voltages: $V_A = -4.3 \text{ V}$, $V_B = -0.7 \text{ V}$,
 $V_C = +0.7 \text{ V}$, $V_D = 0 \text{ V}$, $V_E = +3.6 \text{ V}$,
 $V_F = +4.3 \text{ V}$, $V_G = +4.3 \text{ V}$

(b)

Transistor	I_C (mA)	g_m (mA/V)	r_o (M Ω)
Q_1	0.1	4	2
Q_2	0.1	4	2
Q_3	0.1	4	2
Q_4	1.0	40	0.2

(b) Contd.

Transistor	I_C (mA)	g_m (mA/V)	r_o (M Ω)
Q_5	0	0	∞
Q_A	0.1		
Q_B	0.2		
Q_C	0.1		2
Q_D	1.0		0.2
Q_E	0.1		
Q_F	0.1		
Q_G	0.2		1

(c) Total resistance at collector Q_3

$$\approx \beta_3 r_{o3} \parallel r_{o5} \parallel (\beta_4 + 1)(r_{o4} \parallel r_{o6})$$

$$= 100 \times 2 \parallel 2 \parallel 101(0.2 \parallel 0.2)$$

$$= 1.65 \text{ M}\Omega$$

$$\frac{V_{o3}}{V_i} = +g_{m1} \times \frac{1}{2} \times 1.65 \times 10^3$$

$$= 3300 \text{ V/V}$$

$$\frac{V_{o3}}{V_{o2}} \approx 1$$

Thus, $\frac{V_{o3}}{V_i} \approx 3300 \text{ V/V}$ (polarity correct)

(d) $R_{in} = 2 r_{\pi 1}$

$$= 2 \times \frac{1000}{4} = 50 \text{ k}\Omega$$

$$R_{out} = r_{oD} \parallel r_{o4} \parallel \left[r_{e4} + \frac{r_{o3} \parallel (\beta_3 r_{o3})}{\beta + 1} \right]$$

$$= 0.2 \parallel 0.2 \parallel \left[25 \times 10^{-6} + \frac{2 \parallel 100 \times 2}{101} \right]$$

$$\approx 16.4 \text{ k}\Omega$$

(e) $V_{ICM} |_{min} = -4.3 - 0.4 + 0.7 = -4 \text{ V}$

$$V_{ICM} |_{max} = V_G + 0.4 = +4.7 \text{ V}$$

(f) The voltage at the base of Q_4 can rise to $V_{B3} (V_E) + 0.4 = +4 \text{ V}$. Thus V_O can go up to $+3.3 \text{ V}$


The voltage at the output can go down to $V_{Base} \text{ of } Q_D + 0.4 = V_A + 0.4 = -4.3 - 0.4 = -4.7 \text{ V}$

Thus the linear range at the output is $-4.7 \text{ V to } +3.3 \text{ V}$

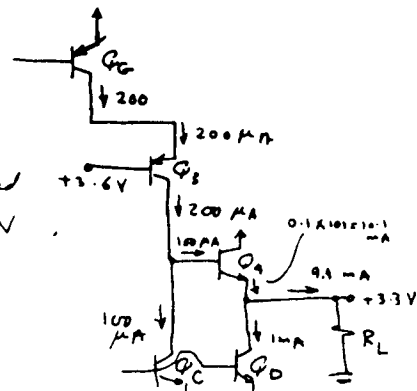(g) At the positive limit of V_O , i.e. $V_O = +3.3 \text{ V}$ and Q_2 just cut off

$$R_L = \frac{3.3 \text{ V}}{9.1 \text{ mA}} = 363 \Omega$$

(This is the minimum allowed R_L for $+3.3 \text{ V}$ output)



At the negative limit of V_O , i.e. $V_O = -3.3 \text{ V}$ and Q_1 has cut off. Q_3 also will be cut off, and Q_4 will cut off.

Thus $R_L = \frac{4.7}{11.1 \text{ mA}} = 423 \Omega$

This is the minimum allowed R_L for a -4.7 V output.

