
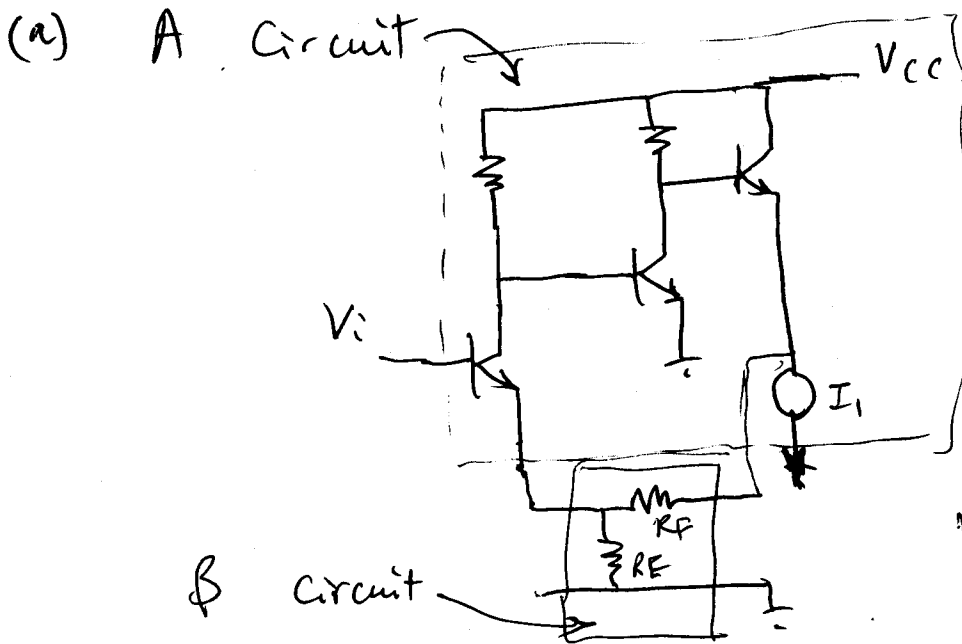


ECE414 Fall 2003 Quiz 4 (open book)	Name	
	Mark	/ 25

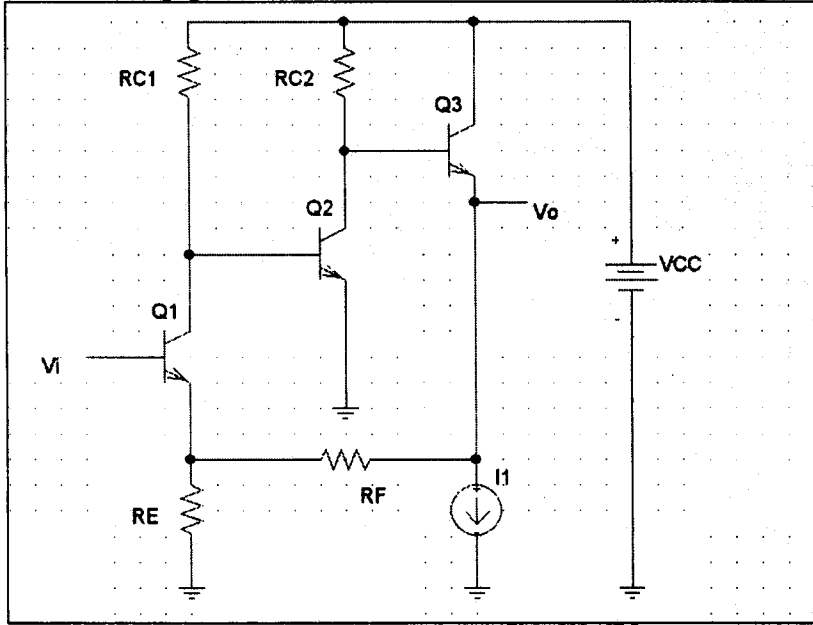1. For the common emitter amplifier below,  $R_E=100$  ohms,  $R_F=1.5k$  ohm. (10 points)  
(a) Draw the A circuit and the  $\beta$  circuit separately. Find the expression for  $\beta$ .  
(b) Find approximate closed loop gain. Assume  $A=5000$



$$V_f = \beta V_o = \frac{R_E}{R_F + R_E} V_o$$

$$\beta = \frac{R_E}{R_F + R_E} = 0.0625$$

(b)  $A_f = \frac{A}{1 + A\beta} = \frac{5000}{1 + 5000 \cdot \beta}$

$$= 15.9$$

or  $A_f \approx \frac{1}{\beta} \approx 16$

2. An amplifier has midband gain of  $10^7$  and three poles at the same location  $10^6$  rad/s, find the value of  $\beta_{min}$  so that closed loop control is stable, assume  $\beta$  is frequency independent. Find the corresponding closed loop midband gain for  $\beta = 0.1\beta_{min}$ . What is the frequency of the closed loop pole corresponding to the open loop dominate pole at  $\beta_{min}$  (15 points).

(a)  $A(s) = \frac{10^7}{(1 + \frac{s}{10^6})^3}$

(9)  $\varphi = -3 \tan^{-1} \frac{\omega}{10^6}$   
 when  $\varphi = -180^\circ$ ,  $|A\beta| \geq 1$  unstable

$-3 \tan^{-1} \frac{\omega}{10^6} = -180^\circ$ ,  $\omega = \sqrt{3} \times 10^6$  rad/s.

$|A\beta| = \frac{10^7}{(1 + \frac{\sqrt{3} \times 10^6}{10^6})^{3/2}} \beta \geq 1$ ,  $\frac{10^7}{8} \beta \geq 1$

$\beta_{min} = 8 \times 10^{-7}$  for system unstable  
 or  $\beta < 8 \times 10^{-7}$  to make feed back stable

(4) (b)  $\beta = 0.1 \beta_{min} = 0.8 \times 10^{-7}$   
 $A_{f_m} = \frac{A}{1 + A\beta} = \frac{10^7}{1 + 0.8 \times 10^{-7} \times 10^7} = 0.56 \times 10^7$

(2) (c)  $A_f(s) = \frac{A(s)}{1 + A(s)\beta_{min}}$ , new pole.  $1 + A(s)\beta_{min} = 0$   
 $1 + 8 \times 10^{-7} \frac{10^7}{(1 + \frac{s}{10^6})^3} = 0$ .  $(1 + \frac{s}{10^6})^3 = -8$ ,  $1 + \frac{s}{10^6} = -2$   
 $s = -3 \times 10^6$  rad/s. 3 - new pole at  $3 \times 10^6$  rad/s